

**PSG COLLEGE OF TECHNOLOGY**  
**(AUTONOMOUS INSTITUTION)**  
**COIMBATORE-641 004**



**TOPIC: RL HIGH PASS FILTER FREQUENCY  
AND TIME DOMAIN ANALYSIS**

**BRANCH: ELECTRONICS AND  
COMMUNICATION ENGINEERING**

**SUBJECT: CONTROL SYSTEM**

**SUBJECT CODE: 19L504**

**SUBMITTED BY: SANGEETHA-21L416**

**MERUSHETHA-21L408**

**YOGASELVAMUTHU-21L418**


**SHEENA S-20L141**

## MANUAL CALCULATION:

### 1 MANUAL CALCULATION:-

(A) Derive the Transfer Function of the Circuit

CIRCUIT DIAGRAM.

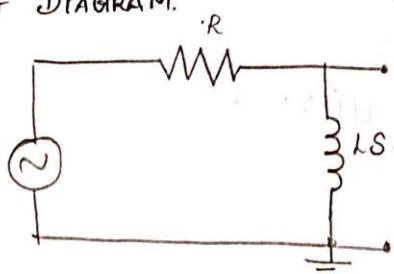

Designing  $RL$  high pass filter for cut-off frequency  $2\text{kHz}$ .

$$f = \frac{R}{2\pi L}$$

$$\text{Let } R = 500\text{ mH}$$

$$R = 6.3\text{ k}\Omega$$

$$\frac{R}{L} = 12600$$

By Voltage Divider Rule,

$$V_o = \frac{Ls}{Ls + R} \times V_i$$

$$\frac{V_o}{V_i} = \frac{s}{s + R/L} \Rightarrow \frac{s}{s + 12600}$$

(B) IMPULSE RESPONSE OF THE SYSTEM.

$$\frac{Y(s)}{X(s)} = \frac{s}{s + 12600}$$

$$H(s) = \frac{s}{s + 12600}$$

$$\frac{s}{s + 12600} = \frac{A}{s + 12600} + \frac{B}{s + 12600}$$

$$L^{-1}(H(s)) = L^{-1}\left(1 - \frac{12600}{s + 12600}\right)$$

$$= S(t) - 12600 e^{-12600t} u(t)$$

(c) Output of the system for some standard input

Let the standard input be unit step response,

$y(s) = X(s) \times \text{Transfer Function}$ ,

$$Y(s) = \frac{1}{s} \times \frac{s}{s + 12600}$$

$$= \frac{1}{s + 12600}$$

$$y(t) = e^{-12600t} u(t)$$

$$y(t) = \begin{cases} e^{-12600t}, & u(t) > 0 \\ 0, & \text{otherwise.} \end{cases}$$

D Analyse the stability of the system by RH Criterion:

$$\text{Transfer Function} = \frac{s}{s + 12600} \quad \text{No. of poles} = 1$$

$$\text{No. of zeros} = 0$$

Poles

$$s = -12600, \text{ Pole lies in the LHS, so}$$

the system is stable.


$$s^1: 1 \quad \left. \begin{array}{l} \text{no sign change} \\ \hline \end{array} \right\}$$

$$s^0: 12600$$

(E) Perform Time response analysis of the System.

Transfer Function =  $\frac{s}{s+12600}$

$s+12600$ .

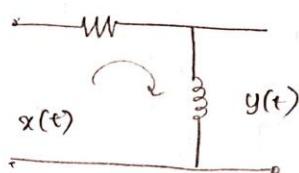

$$T(s) = \frac{s}{s+R/L} = \frac{s}{s+\frac{1}{T}}$$

Applying KVL

$$x(t) = R i(t) + y(t)$$

$$i(t) = \frac{1}{L} \int y(t) dt$$

differential Equation for 1st order system  $\Rightarrow x(t) = \frac{R}{L} \int y(t) dt + y(t)$

taking Laplace Transform

$$X(s) = \frac{R}{Ls} Y(s) + Y(s)$$

$$\frac{Y(s)}{X(s)} = \frac{Ls}{Ls+R} \Rightarrow \frac{s}{s+R/L} \Rightarrow \frac{s}{s+12600}$$

$$\boxed{G_1(s) = \frac{s}{12600}}$$

i) Unit step response of 1st order system.

$$T(s) = \frac{C(s)}{R(s)} = \frac{s}{s+12600}$$

Input is  $r(t) = u(t)$ .

$$\text{Laplace transform } (r(t) = \frac{1}{s}) = R(s)$$

$$C(s) = R(s) \times \frac{s}{s+12600}$$

$$C(s) = \frac{1}{s} \times \frac{s}{s+12600}$$

$$\Rightarrow \frac{1}{s+12600} = \underline{\underline{A}}$$

taking inverse Laplace Transform,


$$\boxed{C(t) = \frac{-12600t}{e^{12600t}} u(t)} = \begin{cases} e^{-12600t}, & u(t) > 0 \\ 0, & \text{otherwise.} \end{cases}$$

$$C_{sf}(t) = 0. \quad C_{tr} = e^{-12600t}$$

$$c(t) = e^{-12600t} = e^{-R/L t} = e^{-\frac{1}{(RL)} t} = e^{-t/T}$$

For  $t > 0$ .

$t$	0	$T$	$2T$	$3T$	$4T$	$5T$	
$c(t)$	1	0.367	0.135	0.049	0.0183	0.006	

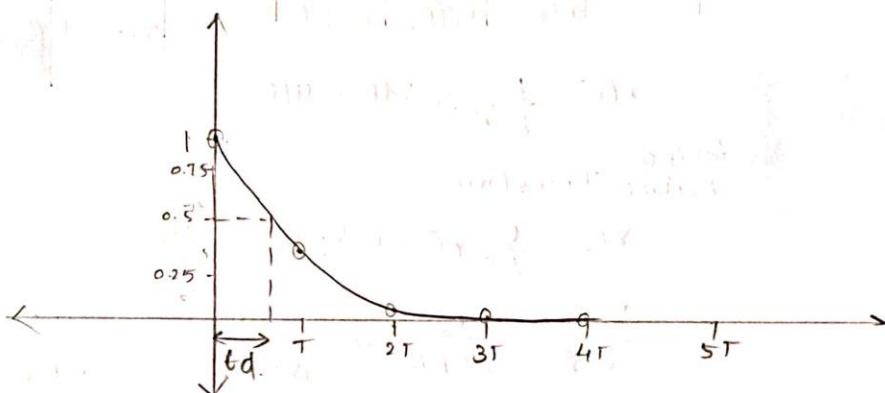

$t_d$  (delay time)

$$c(t) = 0.5 \\ 0.5 = e^{-12600t}$$

~~-0.693~~

$$-0.693 = -12600 t$$

$$0.055 \text{ ms} = t_d.$$

$$t_d = 0.055 \text{ ms.}$$

Time constant  $T$ ,

$$\text{at } t = T, c(t) = e^{-1} = 0.367.$$



## (2) UNIT RAMP RESPONSE OF THE FIRST ORDER SYSTEM.

When input is unit ramp function,

$$r(t) = t u(t)$$

$$R(s) = \frac{1}{s^2}$$

$$C(s) = R(s) \times \frac{s}{s + R/L}$$

$$= R(s) \times \frac{1}{s(s + R/L)}$$

$$= \frac{1}{s(s + R/L)} = \frac{A}{s} + \frac{B}{s + R/L}$$


$$= \frac{L}{R} \left( \frac{1}{s} \right) + -\frac{L}{R} \left( \frac{1}{s + R/L} \right)$$

$$L^{-1} = \frac{L}{R} u(t) - \frac{L}{R} e^{-R/L t} u(t)$$

$$= T - T e^{-t/T}$$

$$\boxed{c(t) = T(1 - e^{-t/T})} \text{ for } u(t) > 0.$$

$t$	0	$T$	$2T$	$3T$	$4T$	$5T$	$6T$	$7T$
$c(t)$	0	<del><math>1.000T</math></del>	<del><math>0.632T</math></del>	<del><math>0.86T</math></del>	<del><math>0.95T</math></del>	<del><math>0.981T</math></del>	<del><math>0.99T</math></del>	$0.99T$

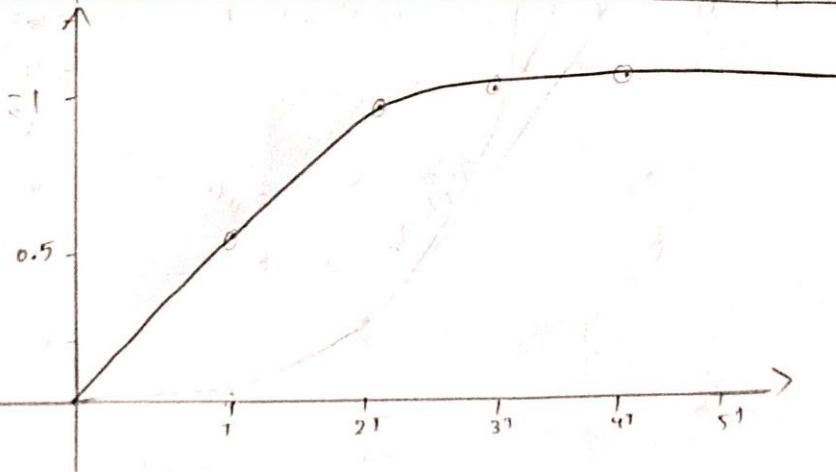

Unit parabolic response of first order system -

$$R(t) = \frac{t^2}{2} u(t)$$

$$R(s) = \frac{1}{s^3}$$

$$C(s) = \frac{1}{s^2} \times \frac{s}{s + R/L}$$

$$= \frac{1}{s^2(s + R/L)} = \frac{A}{s^2} + \frac{B}{s} + \frac{C}{s + R/L}$$

After solving we get,

$$A = T, B = -T^2, C = T^2.$$


$$C(s) = T\left(\frac{1}{s^2}\right) - T^2\left(\frac{1}{s}\right) + T^2\left(\frac{1}{s+R/L}\right)$$

$$= T R(t) - T^2 u(t) + T^2 e^{-t/T} u(t)$$

$$= T \cdot t u(t) - T^2 u(t) + T^2 e^{-t/T} u(t)$$

$$\boxed{C(t) = (tT - T^2 + T^2 e^{-t/T})} \quad \text{for } u(t) > 0.$$

$t$	0	$T$	$2T$	$3T$	$4T$	$5T$
$C(t)$	0.	$0.36T^2$	$1.135T^2$	$2.049T^2$	$3.018T^2$	$4.006T^2$

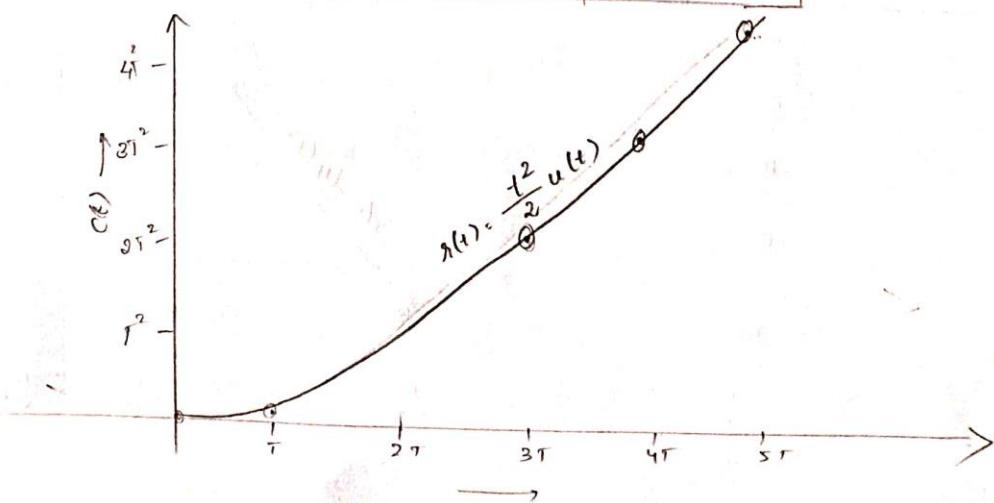

(ii) Unit Impulse response  $r(t) = \delta(t)$   $R(s) = 1$

$$C(s) = \frac{s}{s + R/L}$$

$$c(t) = L^{-1} \left( \frac{s}{s + R/L} \right)$$


$$= \delta(t) - \frac{R}{L} e^{-R/L t}$$

$$\boxed{c(t) = \delta(t) - \frac{1}{T} e^{-t/T}}$$

$t$	0	$T$	$2T$	$3T$	$4T$
$c(t)$	$\delta(t) - \frac{1}{T}$	$\delta(t) - \frac{0.367}{T}$	$\delta(t) - \frac{0.135}{T}$	$\delta(t) - \frac{0.049}{T}$	$\delta(t) - \frac{0.018}{T}$

if  $\delta(t)=0$ ,

$T=1$ .

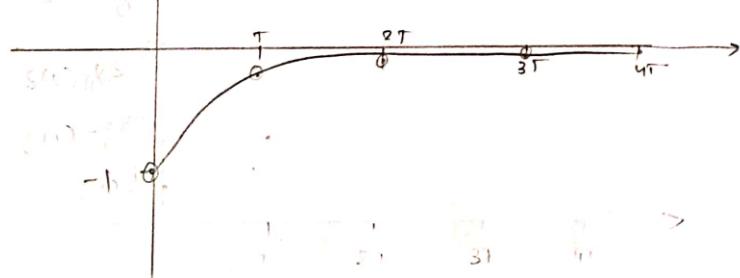


$r(t)$	$c(t)$
Unit step, : $u(t)$	$e^{-t/T}$
Unit ramp : $t u(t)$	$T(1 - e^{-t/T})$
Unit parabola : $\frac{t^2}{2} u(t)$	$tT - T^2 + T^2 e^{-t/T}$
Unit impulse : $\delta(t)$	$\delta(t) - \frac{1}{T} e^{-t/T}$

# SIMULATION OF THE CIRCUIT:


SOFTWARE USED: MULTISIM:

CUT-OFF FREQUENCY=2KHZ

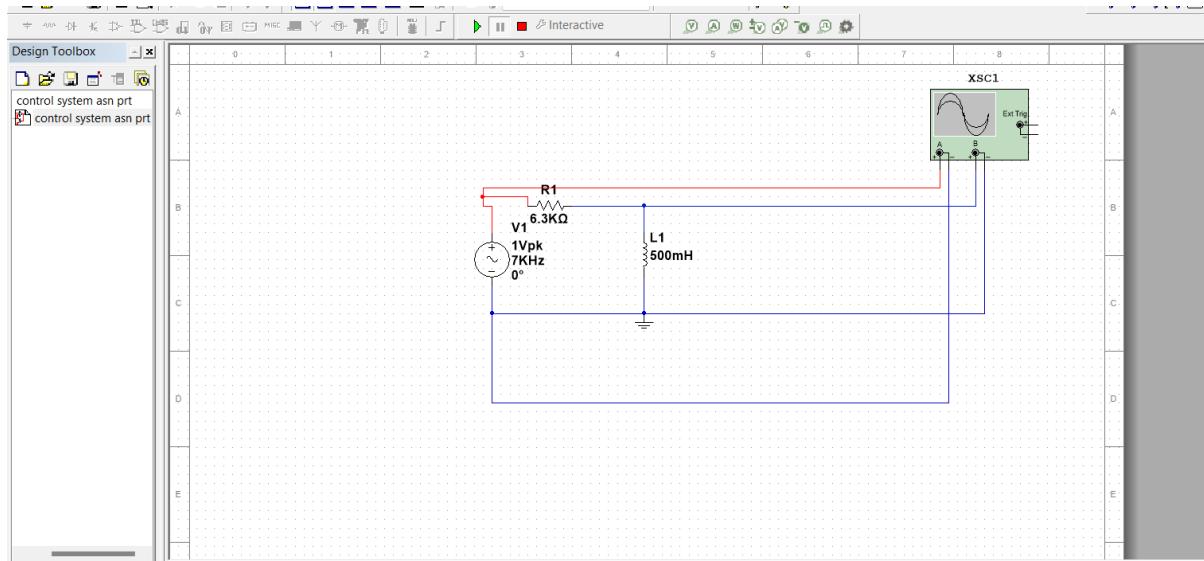


WHEN FREQUENCY <2KHZ

VOUT(P-P)=0.48V VIN(P-P)=2V

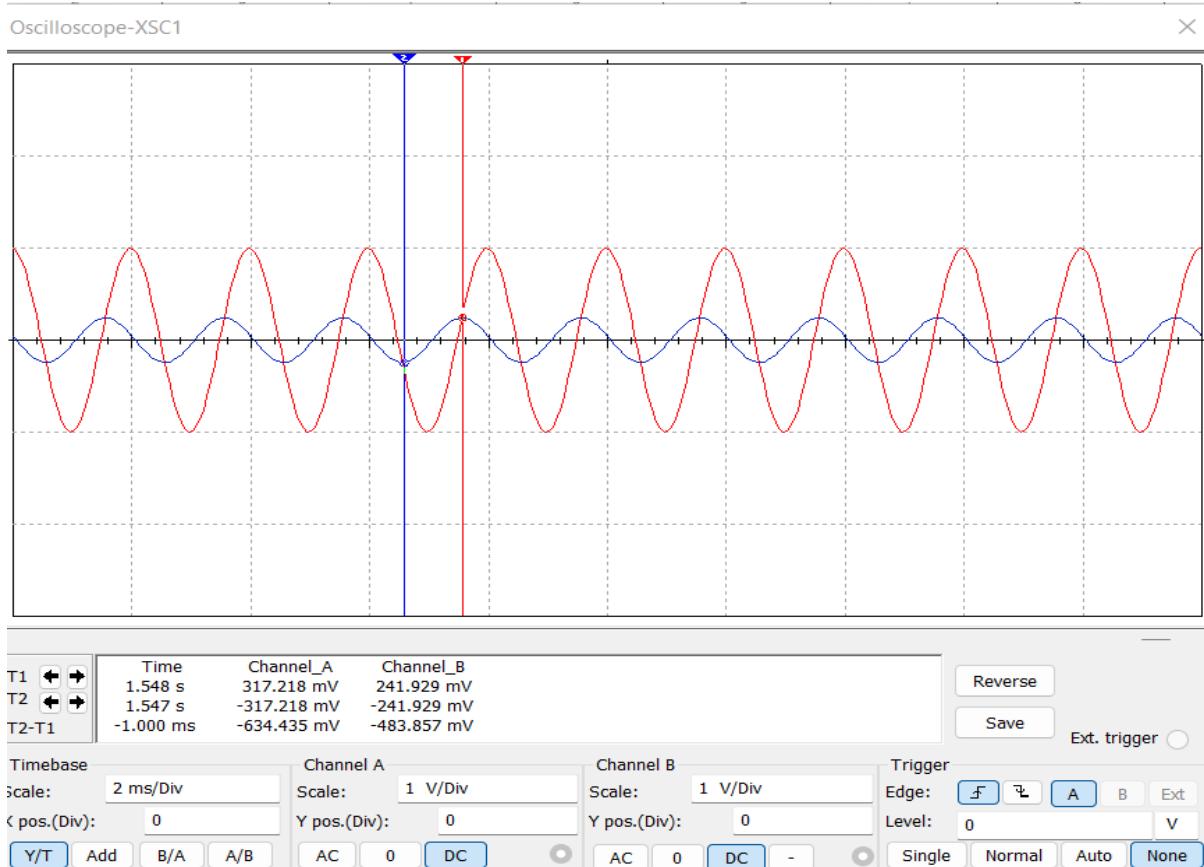
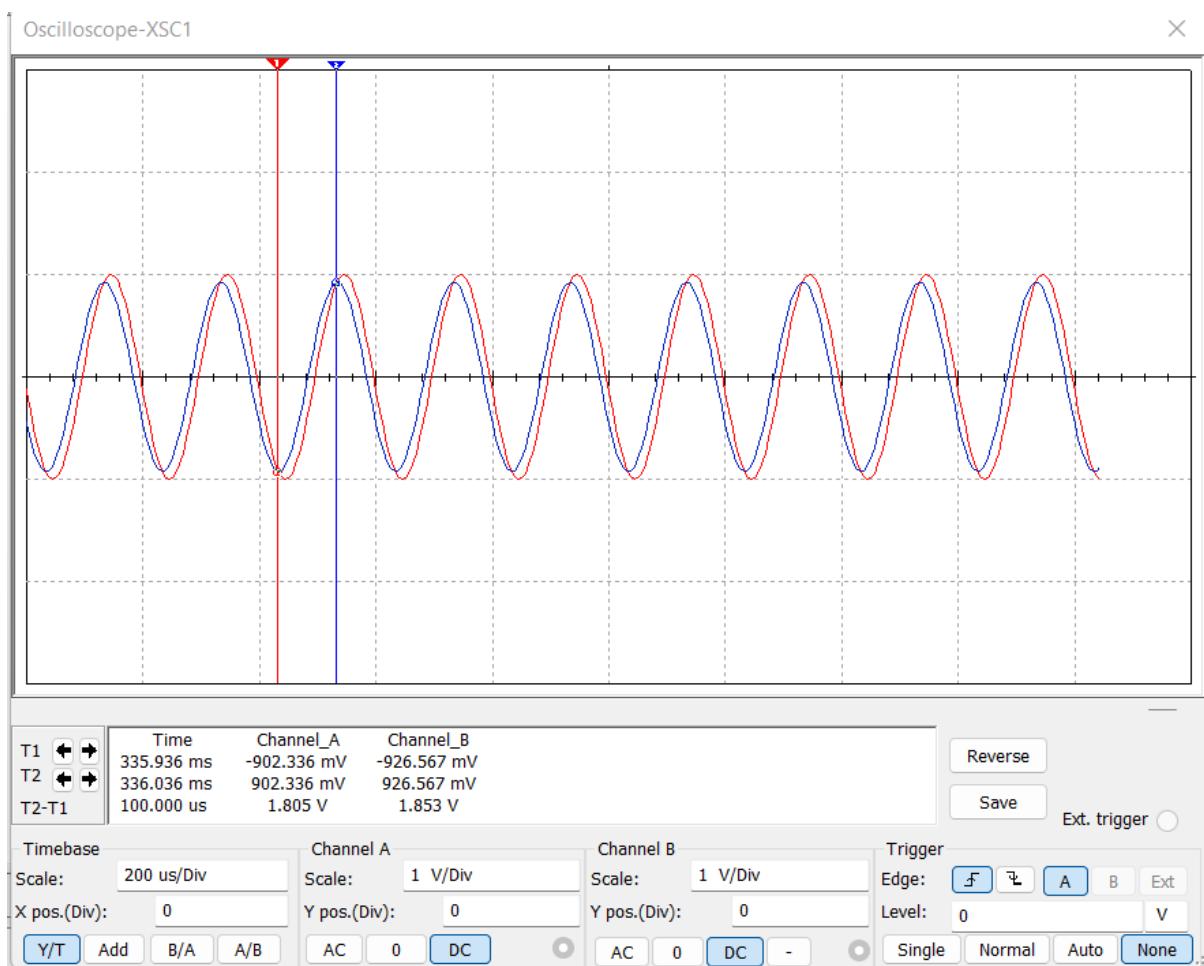
## WHWN FREQUENCY >2KHZ

V<sub>OUT</sub>(P-P)= 1.85V V<sub>IN</sub>(P-P)= 2V



## MATLAB IMPLEMENTATION:


Code:

```
I=tf([1,0],[1,12600]);%defining transfer function
subplot(421);
bode(I); %bode plot
subplot(422);
nyquist(I); %nyquist plot
subplot(423);
rlocus(I); %root locus
[a,b]=bode(I)
b=b(1,:);
a=a(1,:);
subplot(424); %polar plot
polar(b*pi/180,a);
title('polar plot');

disp(I);
%time response analysis
R=6300;
L=0.5;
T=L/R;
%unit step function
c=1;s=[];
for t=0:1:10
    s(c)=exp(-t*(1/T));
    c=c+1;
end
t=0:1:10;
subplot(425);
plot(t,s);
title('unit step response');
%unit ramp
c=1;s=[];
for t=0:1:10
    s(c)=T*(1-exp(-t*(1/T)));
    c=c+1;
end
t=0:1:10;
subplot(426);
plot(t,s);
title('unit ramp response');

%unit parabolic
c=1;s=[];
for t=0:0.1:10
    s(c)=t*T-(T*T)+((T*T)*exp(-t*(1/T)));
    c=c+1;
end
t=0:0.1:10;
subplot(427);
plot(t,s);
title('unit parabolic response');
```

## OUTPUT:

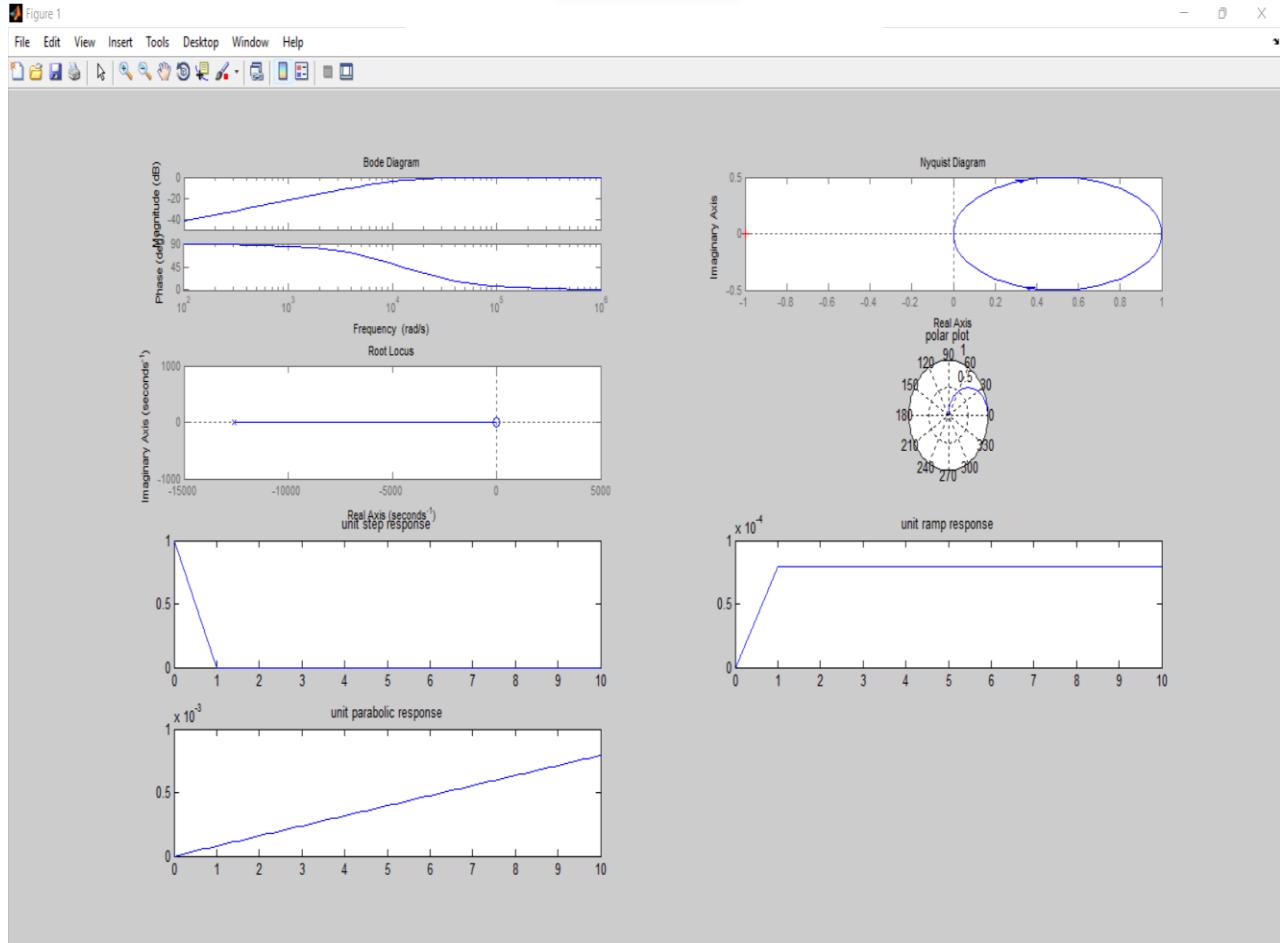

The system is stable.

## CONCLUSION:

Thus time response analysis and frequency response analysis for RL high pass filter is been done and polar,Nyquist ,bode and time response plots have been done using matlab.