




ASSIGNMENT PRESENTATION

BY S.SHEENA

201141



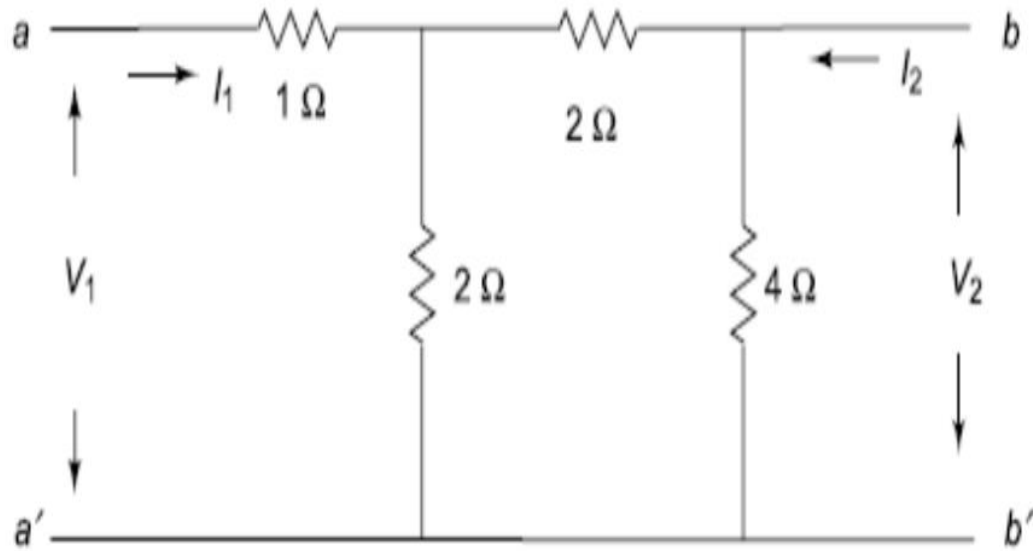Determine the Z parameter for the given network



- $v_1 = z_{11}I_1 + z_{12}I_2$
- $v_2 = z_{21}I_1 + z_{22}I_2$
- $Z_{11} = \left. \frac{v_1}{I_1} \right|_{I_2=0}$ open circuit input impedance
- $Z_{21} = \left. \frac{v_2}{I_1} \right|_{I_2=0}$ open circuit forward transfer impedance
- $Z_{12} = \left. \frac{v_1}{I_2} \right|_{I_1=0}$ open circuit reverse transfer impedance
- $Z_{22} = \left. \frac{v_2}{I_2} \right|_{I_1=0}$ open circuit output impedance

- When $I_2 = 0$ (open circuiting bb')

$$Z_{11} = \frac{v_1}{I_1} \quad \text{to find } v_1,$$

$$v_1 = R_{eq} \times I_1$$


$$R_{eq} = 1 + [2 \parallel (2+4)]$$

$$= 1 + \frac{2 \times 6}{2+6}$$

$$= \frac{5}{2}$$

$$v_1 = \frac{5}{2} I_1$$
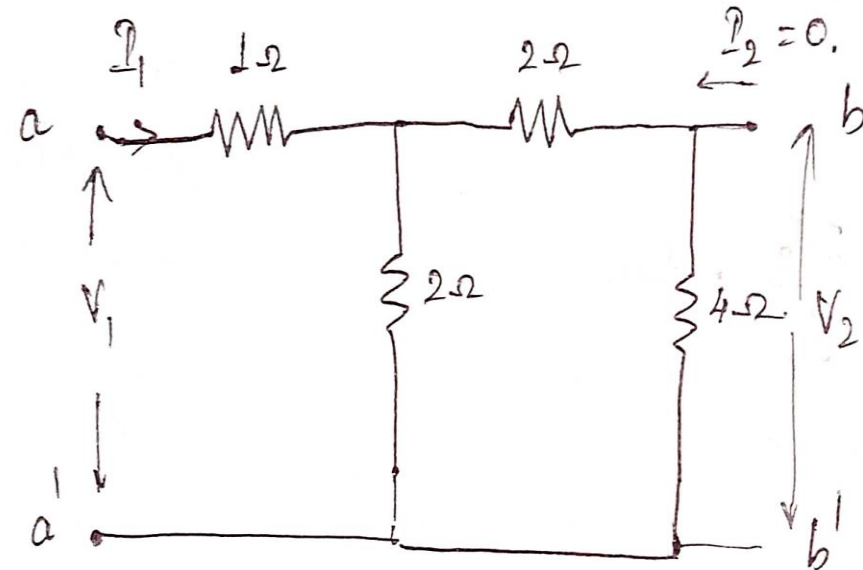
$$Z_{11} = \frac{v_1}{I_1} = \frac{\frac{5}{2} I_1}{I_1} = 2.5 \Omega$$



- $Z_{21} = \frac{v_2}{I_1}$
- To find v_2 :

v_2 is the voltage across 4Ω


by current division method

$$v_2 = 4 \times I_{2\Omega, 4\Omega} \qquad I_{2\Omega, 4\Omega} = \frac{2}{8} I_1$$

$$v_2 = 4 \times \frac{I_1}{4} \qquad = \frac{I_1}{4}$$

$$v_2 = I_1$$
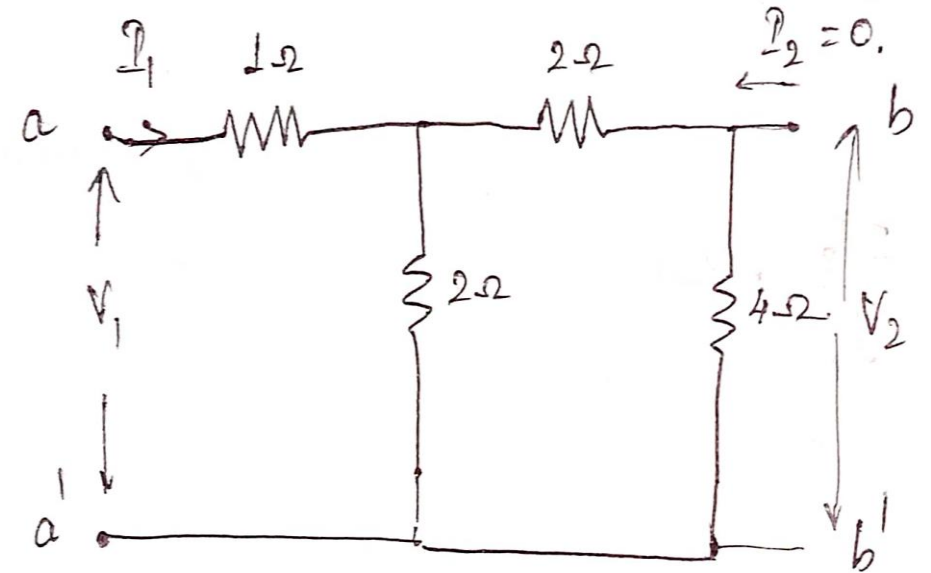
$$Z_{21} = \frac{v_2}{I_1} = \frac{I_1}{I_1} = 1\Omega$$



- When $I_1 = 0$ (open circuiting aa')

- $Z_{12} = \frac{v_1}{I_2}$

v_1 is voltage across 2Ω


$$v_1 = 2\Omega \times I_{2\Omega, 2\Omega}$$

$$v_1 = 2 \times \frac{1}{2} I_2 = I_2$$


$$Z_{12} = \frac{v_1}{I_2} = \frac{I_2}{I_2} = 1\Omega$$

by current division :
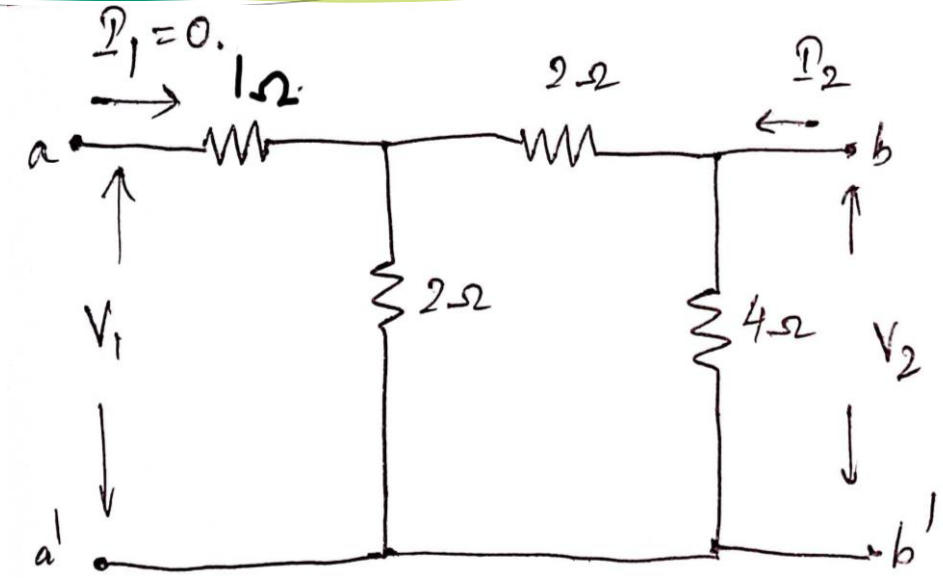
$$I_{2\Omega, 2\Omega} = \frac{4}{8} I_2 = \frac{1}{2} I_2$$



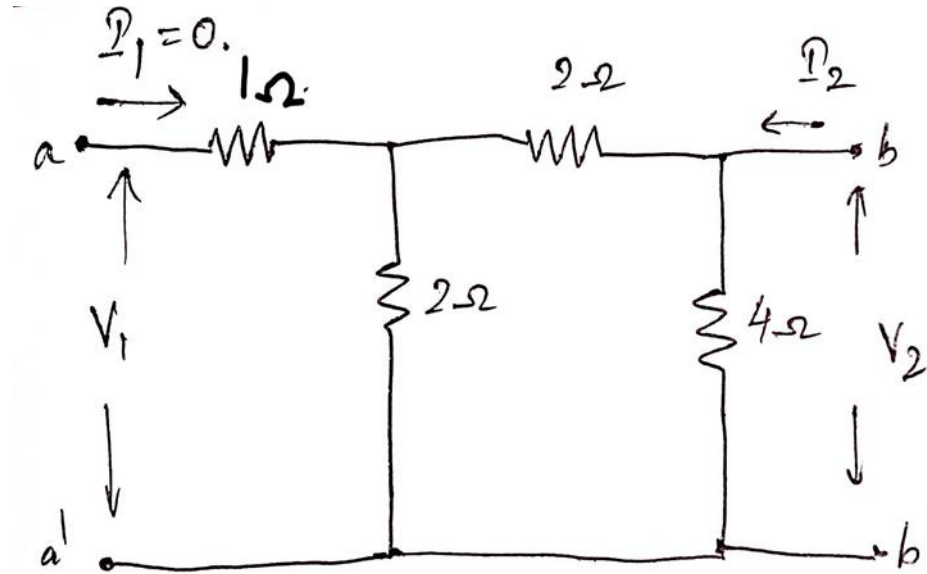- $Z_{22} = \frac{v_2}{I_2}$
- $v_2 = I_2 \times R_{eq}$
 $= I_2 \times \left(\frac{4 \times 4}{4 + 4} \right) = \frac{16}{8} I_2$
 $= 2 \times I_2$
- $Z_{22} = \frac{v_2}{I_2} = \frac{2I_2}{I_2} = 2\Omega$



In this circuit, $Z_{12} = Z_{21} = 1\Omega$, this network is a reciprocal network



Thank you