

7.2. Prove that the Q of the circuit shown in Fig. 7.32(a) is given by Eq. (7.62).

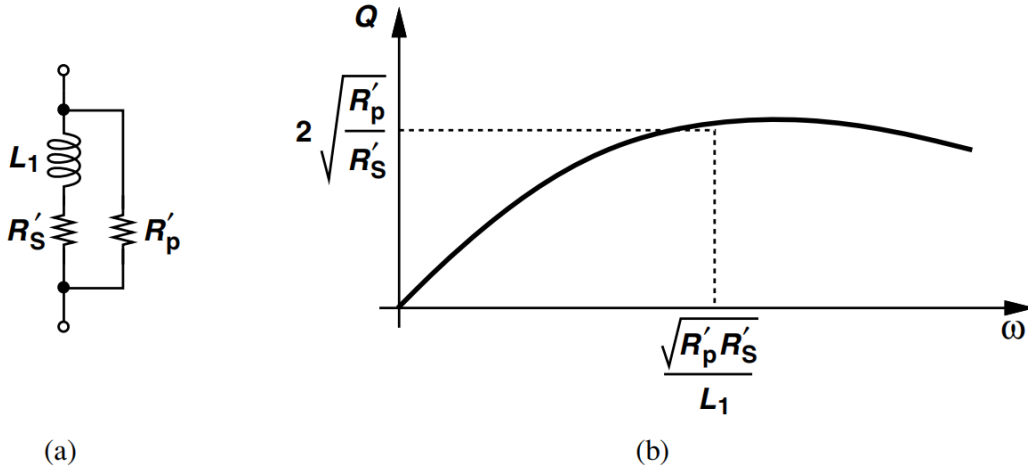


Figure 7.32 (a) Modeling loss by both series and parallel resistors, (b) resulting Q behavior.

$$Q = \frac{L_1 \omega R'_p}{L_1^2 \omega^2 + R'_S (R'_S + R'_p)}. \quad (7.62)$$

7.4. Using Eq. (7.62), compare the Q 's of the circuits shown in Figs. 7.37(b) and (d).

$$Q = \frac{L_1 \omega R'_p}{L_1^2 \omega^2 + R'_S (R'_S + R'_p)}. \quad (7.62)$$

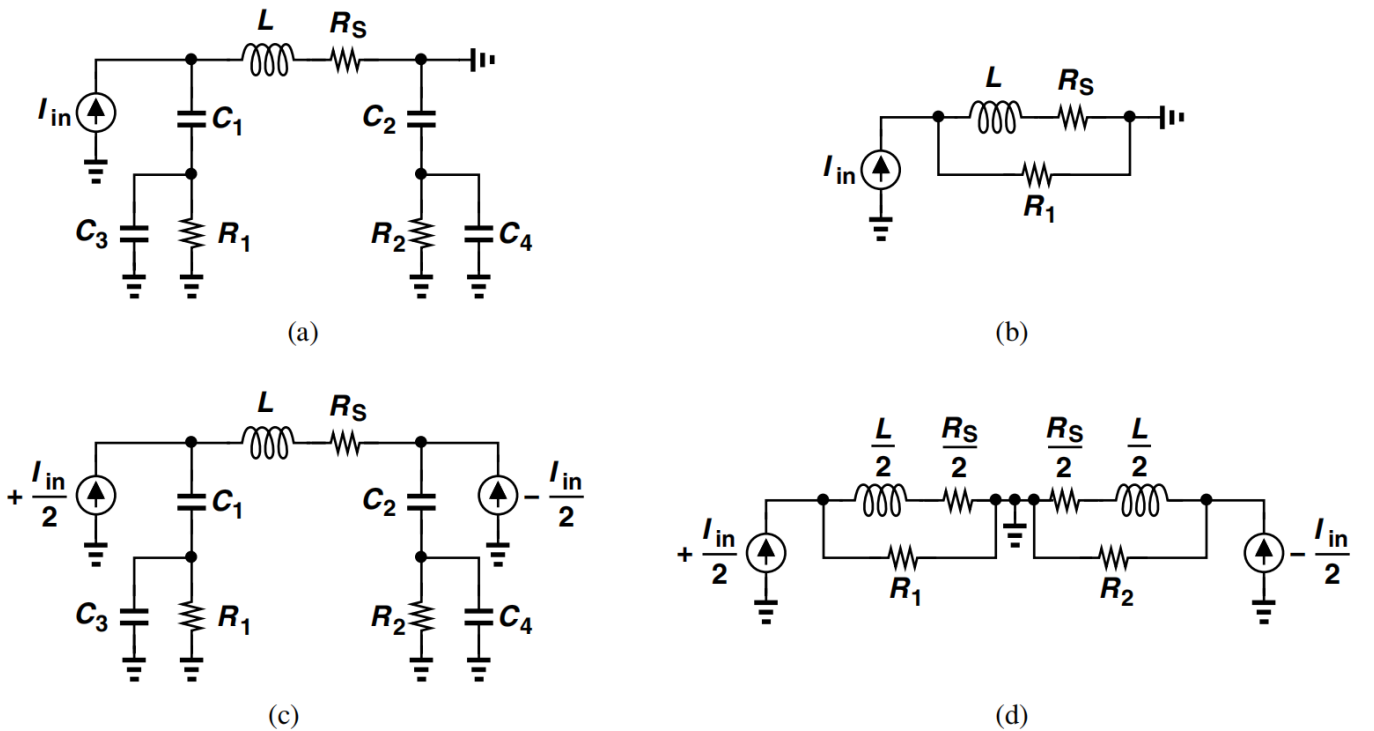


Figure 7.37 (a) Inductor driven by a single-ended input, (b) simplified model of (a), (c) symmetric inductor driven by differential inputs, (d) simplified model of (c).

7.3. Prove that for an N -turn spiral inductor, the equivalent interwinding capacitance is given by

$$C_{eq} = \frac{C_1 + \cdots + C_{N^2-1}}{(N^2 - 1)^2}. \quad (7.125)$$

7.7. For the circuit of Fig. 7.28(a), compute Y_{11} and find the parallel equivalent resistance. Is the result the same as that shown in Eq. (7.55)?

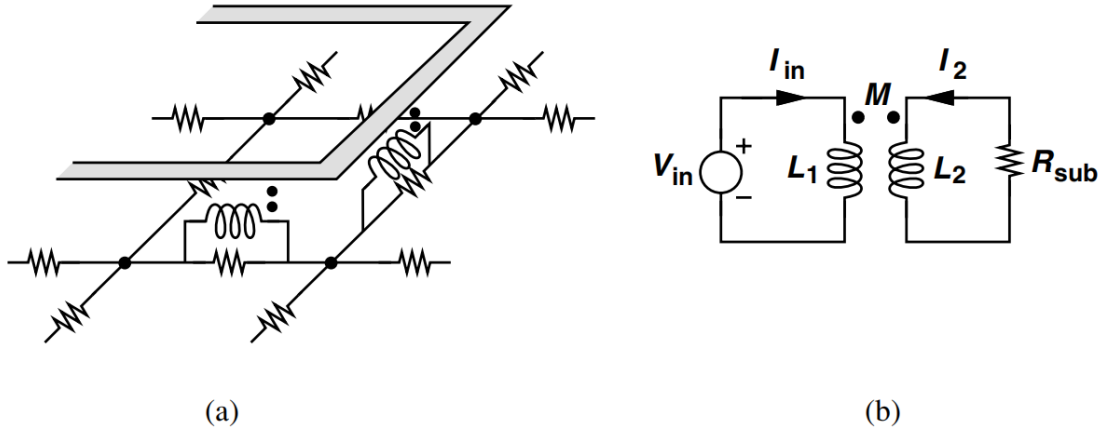


Figure 7.28 (a) Modeling of magnetic coupling by transformers, (b) lumped model of (a).

$$\frac{V_{in}}{I_{in}} = \frac{M^2 \omega^2 R_{sub}}{R_{sub}^2 + L_2^2 \omega^2} + \left(L_1 - \frac{M^2 \omega^2 L_2}{R_{sub}^2 + L_2^2 \omega^2} \right) j\omega, \quad (7.55)$$

7.9. Find the input impedance, Z_{in} , in Fig. 7.50.

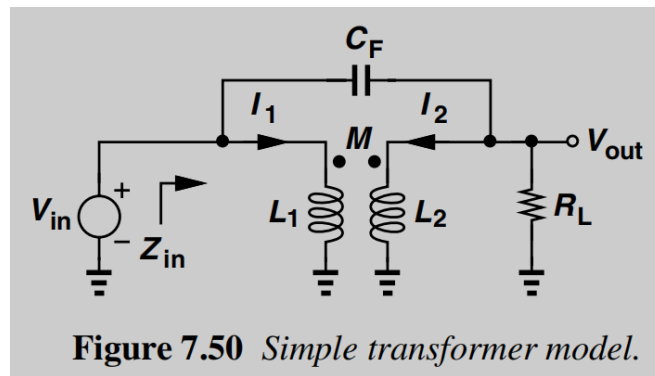


Figure 7.50 Simple transformer model.

7.10. Using the capacitance data in Table 7.1, repeat Example 7.25 for an inductor realized as a stack of four metal layers. Assume the inductance is about 3.5 times that of one spiral.

Example 7.25

Compare the equivalent lumped capacitance of single-layer and stacked 4.96-nH inductors studied in Example 7.23. Assume the lower spiral is realized in metal 5 and use the capacitance values shown in Table 7.1.

Table 7.1 Table of metal capacitances (aF/ μm^2).

	Metal 8	Metal 7	Metal 6	Metal 5	Substrate
Metal 9	52	16	12	9.5	4.4
Metal 8		52	24	16	5.4
Metal 7			88	28	6.1
Metal 6				88	7.1
Metal 5					8.6

Solution:

For a single metal-9 layer, the total area is equal to $2000\ \mu\text{m} \times 4\ \mu\text{m} = 8000\ \mu\text{m}^2$, yielding a total capacitance of 35.2 fF to the substrate. As suggested by Eq. (7.26), the equivalent lumped capacitance is 1/3 of this value, 11.73 fF. For the stacked structure, each spiral has an area of $780\ \mu\text{m} \times 4\ \mu\text{m} = 3120\ \mu\text{m}^2$. Thus, $C_1 = 29.64\ \text{fF}$ and $C_2 = 26.83\ \text{fF}$, resulting in

$$C_{eq} = 12.1\ \text{fF}. \quad (7.80)$$

The choice of stacking therefore translates to comparable capacitances.¹³ If L_2 is moved down to metal 4 or 3, the capacitance of the stacked structure falls more.