

ECEN 607: Advanced Analog Circuit Tech

Lab 1: MOS Device Characterization

Lab Report

Name: FirstName LastName
UIN: ***Last Three Digits**

Objectives:

To review concepts learned in background classes such as characterization, small-signal and CMOS circuit design.

5 V Transistor Characterization

High voltage CMOS design is done in many applications even today. In this course, you will be designing circuits operating both at 1.8 V supply and 5.5 V supply. Using the technology process IBM180 and the following procedure, characterize the four terminal, **5.5 V** nominal, MOS transistors **nfetmx** and **pfetmx**.


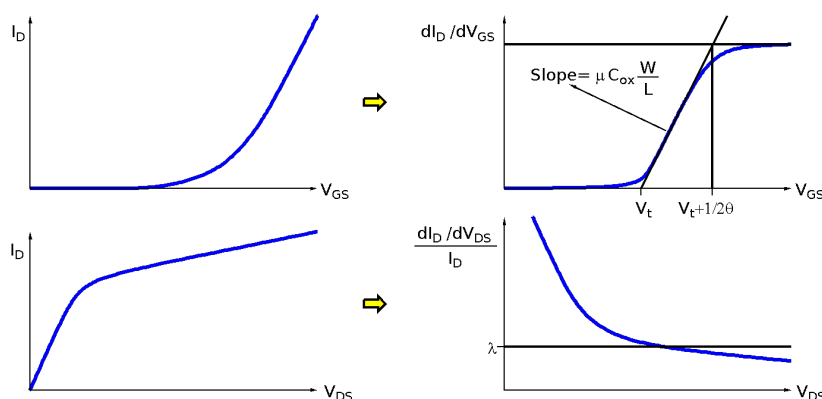



Figure 1-11: Curves used for CMOS characterization

To obtain g_m , derivative of I_D needs to be plotted as a function of V_{GS} . The resulting plot can be used to extract V_t , μC_{ox} and θ , as shown above. Channel length modulation parameter lead to the finite value of the output conductance, and can be extracted by taking the derivative of I_D as a function of V_{DS} .

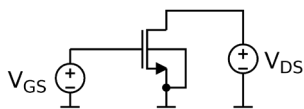1. Construct the circuit below using **nfetmx** transistor with $W/L=1\mu/0.7\mu$.



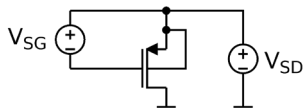- a. Fix $V_{DS}=2V$. Sweep V_{GS} from 0 to 5V, plot I_D and $g_m (dI_D/dV_{GS})$ vs. V_{GS} , and extract V_{tn} , $\mu_n C_{ox}$ and θ .
 - b. Set $V_{GS}=V_{tn}+100mV$. Sweep V_{DS} from 0 to 5V, plot and $g_{ds} (dI_D/dV_{DS})$ vs. V_{DS} . Plot the output resistance r_{ds} , and its first and second derivative as function of V_{DS} .
 - c. Find the intrinsic gain (A_i) and unity-gain frequency (f_t) using AC simulations when $V_{DS}=2V$ and $V_{GS}=V_{tn}+100mV$.
2. Repeat (1) for the **nfetmx** transistor with $W/L=5\mu/0.7\mu$.
 3. Repeat (1) for the **nfetmx** transistor with $W/L=5\mu/1.4\mu$.
 4. Construct the circuit below using **pfetmx** transistor with $W/L=1\mu/0.5\mu$.



- a. $V_{SD}=2V$. Sweep V_{SG} from 0 to 5V, plot I_D and $g_m=dI_D/dV_{SG}$ vs. V_{SG} , and extract V_{tp} , $\mu_p C_{ox}$ and θ .
- b. $V_{SG}=|V_{tp}|+100mV$. Sweep V_{SD} from 0 to 5V, plot and $g_{ds} (dI_D/dV_{SD})$ vs. V_{SD} . Plot the output resistance r_{ds} , and its first and second derivative as function of V_{SD} .

- c. Find the intrinsic gain (A_i) and unity-gain frequency (f_i) using AC simulations when $V_{SD}=2V$ and $V_{SG}=|V_{tp}|+100mV$.
5. Repeat (4) for the **pfetmx** transistor with $W/L=5\mu/0.5\mu$.
6. Repeat (4) for the **pfetmx** transistor with $W/L=5\mu/1\mu$.

In the lab report, include your schematics, plots, annotations, and calculations. Please provide the characterization results in a plots and comment on the results.