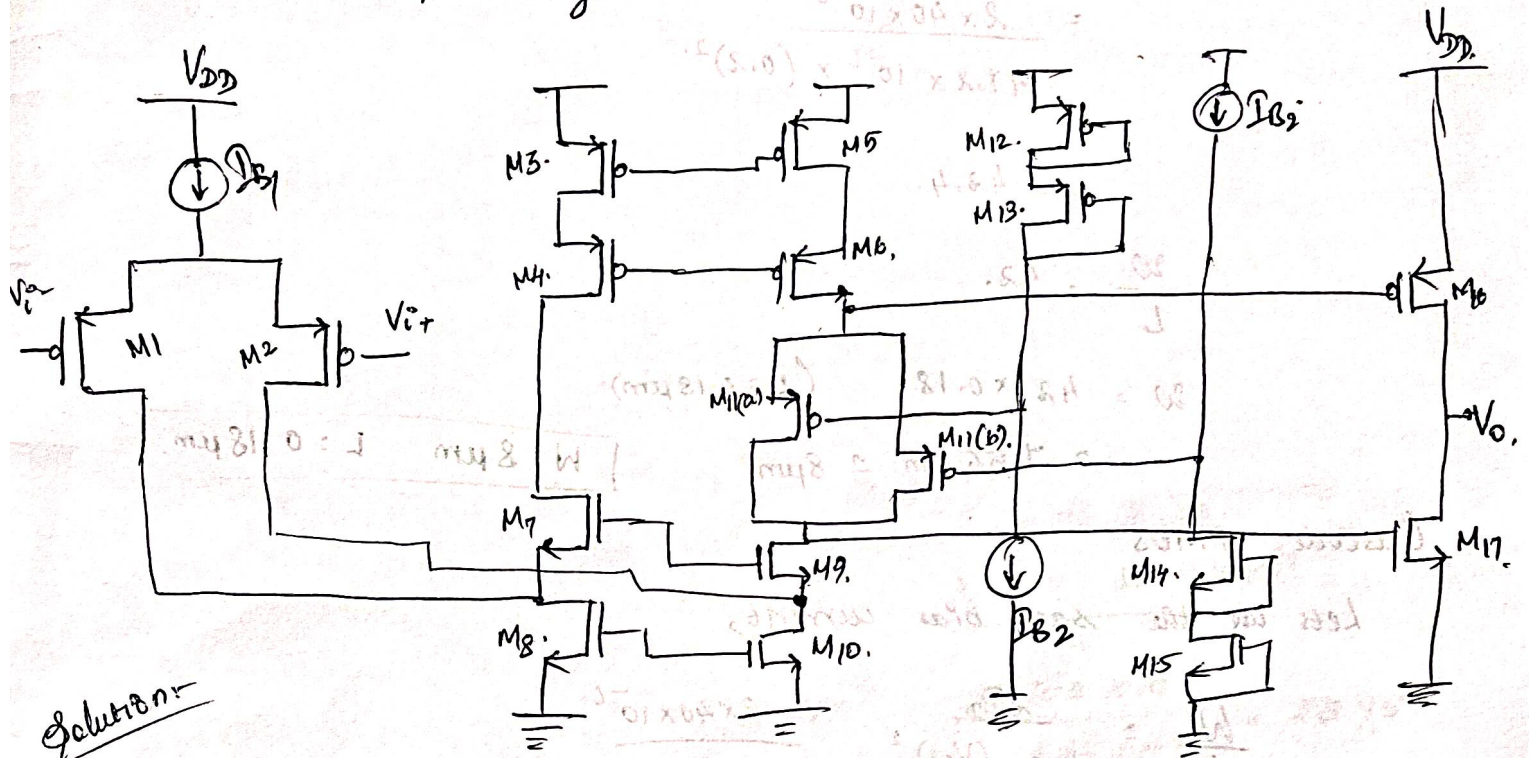


Name : Sheena Selvakumar

UN : 587000654.

Pre-lab : 5 : Two stage folded cascode Op-amp with class AB Output stage.



Solution:-

Considering the following values,

$$\mu_n C_{ox} = 167 \mu A/V^2.$$

$$\mu_p C_{ox} = 47.2 \mu A/V^2.$$

$$V_{ov} = 0.2 V. \text{ (good choice?)}$$

$$V_{DD} = 5 V.$$

$$I_{B1} = 40 \mu A.$$

$$I_{B2} = 40 \mu A.$$

$$I_{B3} = 80 \mu A.$$

$$C_L = 20 pF$$

$$C_C = 5 pF$$

$$\text{Using } L = 0.18 \mu m.$$

Design Specifications:-

$$\text{Supply voltage} = 5 V$$

$$A_{Vo} > 60 dB.$$

$$\text{Slew Rate} = 4 V/\mu s.$$

$$GBW > 10 MHz.$$

$$PM > 45 \text{ deg.}$$

$$\text{Output Swing} = 4.5 V.$$

$$C_L = 20 pF$$

$$\text{Quiescent Power} < 1 mW.$$

Input Pair (PMOS) M_1, M_2 .

$$(\mu_n C_{ox}) = 71.2 \mu A/V^2$$

$$\left(\frac{W}{L}\right) = \frac{2I_D}{\mu_n C_{ox} (V_{ov})^2}$$

$$= \frac{2 \times 40 \times 10^{-6}}{47.2 \times 10^{-6} \times (0.2)^2}$$

$$= 42.4$$

$$\frac{W}{L} = 42$$

$$W = 42 \times 0.18 \quad (L = 0.18 \mu m)$$

$$= 7.56 \mu m \approx 8 \mu m$$

$$\boxed{W = 8 \mu m \quad L = 0.18 \mu m}$$

Cascode PMOS

Let's use the same bias current,

$$\frac{W}{L} = \frac{2I_D}{\mu_n C_{ox} (V_{ov})^2} = \frac{2 \times 40 \times 10^{-6}}{47.2 \times 10^{-6} \times (0.2)^2}$$

$$W = 42.4 \times 0.18$$

$$= 7.56 \mu m$$

$$\approx 8 \mu m$$

Calculate $\frac{W}{L}$ for NMOS M_7, M_9 ,

$$\left(\frac{W}{L}\right)_{7,9} = \frac{2I_D}{\mu_n C_{ox} (V_{ov})^2}$$

$$= \frac{2 \times 40 \times 10^{-6}}{167 \times 10^{-6} \times (0.2)^2} = 12 \times 0.18 \mu m$$

$$= 2.16 \mu m$$

$$\boxed{W = 2.16 \mu m}$$

NMOS Cascode Stacks (M_8, M_{10})

$$\left(\frac{W}{L}\right)_{8,10} = \frac{2 \times 40 \times 10^{-6}}{167 \times 10^{-6} \times (0.2)^2}$$

$$= 11.976$$

$$\approx 12$$

$$W = 2.16 \mu m \quad \text{when } L = 0.18 \mu m$$

For output devices $I_{max} = 80 \mu A$

M_{16} ,

$$\left(\frac{W}{L}\right)_{16} = \frac{2 \times 80 \times 10^{-6}}{47.2 \times 10^{-6} \times (0.2)^2}$$

$$= \frac{160 \times 10^{-6}}{1.888 \times 10^{-6}} = 84.8$$

$$\boxed{W = 15.26 \mu m \quad L = 0.18 \mu m}$$

NMOS, M_{17} ,

$$\left(\frac{W}{L}\right)_{17} = \frac{2 \times 80 \times 10^{-6}}{167 \times 10^{-6} \times (0.2)^2} = \frac{160 \times 10^{-6}}{6.68 \times 10^{-6}} = 23.95$$

$$\boxed{W = 4.31 \mu m \quad L = 0.18 \mu m}$$

For $M_{11(a)}$ and $M_{11(b)}$

$$M_{11(a)} \quad \left(\frac{W}{L}\right)_4 = \frac{2 \times I_{max}}{\mu_n C_{ox} (V_{ov})^2}$$

$$I_{max} = 80 \mu A$$

$$= \frac{2 \times 80 \times 10^{-6}}{167 \times 10^{-6} \times (0.2)^2} = 23.95$$

$$\boxed{W = 4.32 \mu m \quad L = 0.18 \mu m}$$

111 (b).

$$\left(\frac{W}{L}\right)_{M1b} = \frac{2 I_{max}}{\mu_n C_{ox} (V_{ov})^2}$$

$$= \frac{2 \times 80 \times 10^{-6}}{167 \times 10^{-6} \times (0.2)^2}$$

$$= 23.95$$

$$\frac{W}{L} = 24.$$

$$\boxed{W = 4.32 \mu m} \quad \boxed{L = 0.18 \mu m.}$$

Slew Rate

$$SR = \frac{80 \mu A}{20 pF} = 4 V/\mu s.$$

$$Power_{total} = (40 + 40 + 80) \mu A \cdot 5V = 0.8 mW.$$

For first stage, $g_{m1} = \frac{2 I_{D1}}{V_{ov}} = 0.4 mS$

$$r_o = \frac{V_A}{I_{D1}} \approx 500 k\Omega$$

$$A_{v1} \approx 0.4 \cdot 500 k\Omega \approx 200000 > 60 dB.$$

$$GBW = 12.7 MHz \text{ for } C_{DB} = 5 pF.$$

Output swing, with $V_{GS} \approx 0.6V.$

→ easily meets 4.5V swing on 5V rail

Summarizing in a table,

		Function.	W (μm)	L (μm)	β
M1, 2	PMOS	Input diff pairs	7.56	0.18	40 (each)
M3-M6	PMOS	Cascode	7.56	0.18	40
M7-M9	NMOS	Current mirror	2.16	0.18	40
M8-M10	NMOS	Folded cascode sinks	2.16	0.18	40
M11a	PMOS	Class AB Control	15.3 15.3	0.18	80
M11b	NMOS	Class AB Control	15.3 4.32	0.18	80
M12-15	PMOS/NMOS	Bias & Mirror	15.3 μm $\rightarrow$ PMOS 4.32 4 $\rightarrow$ NMOS	0.18	80
M16	PMOS	Output (pull-up)	4.153	0.18	80
M17	NMOS	Output (pull-down)	4.32	0.18	80

For Transistors $\rightarrow$ M13, M12,

$$\beta = 80 \mu$$

M12, M13,

$$\left(\frac{W}{L}\right) = \frac{2 \times 80 \times 10^{-6}}{41.2 \times 10^{-6} \times (0.2)^2}$$

$$= 15.26 \mu\text{m}$$

$$\beta = 80 \mu$$

M14, M15

$$\left(\frac{W}{L}\right) = \frac{2 \times 80 \times 10^{-6}}{167 \times 10^{-6} \times (0.2)^2} = \frac{160 \times 10^{-6}}{6.68 \times 10^{-6}}$$

$$= 23.95$$

$$W = 23.95 \times 0.18$$

$$= 4.31 \mu\text{m}$$

Comments on the compensation techniques.

①. Using Miller compensation,

Adding C_c between output of the 1st stage and the output.

② Using feedforward compensation.

→ Capacitor connecting the first stage output to the output using blocking capacitor, resistor to introduce a path.

(b) Slew - rate mechanism with equations.

$$SR^+ = \frac{40 \mu A}{25 pF} = 1.6 V/\mu s.$$

$$SR^- = \frac{80 \mu A}{25 pF} = 3.2 V/\mu s.$$

Slew rate is set by available stage currents and total output capacitance