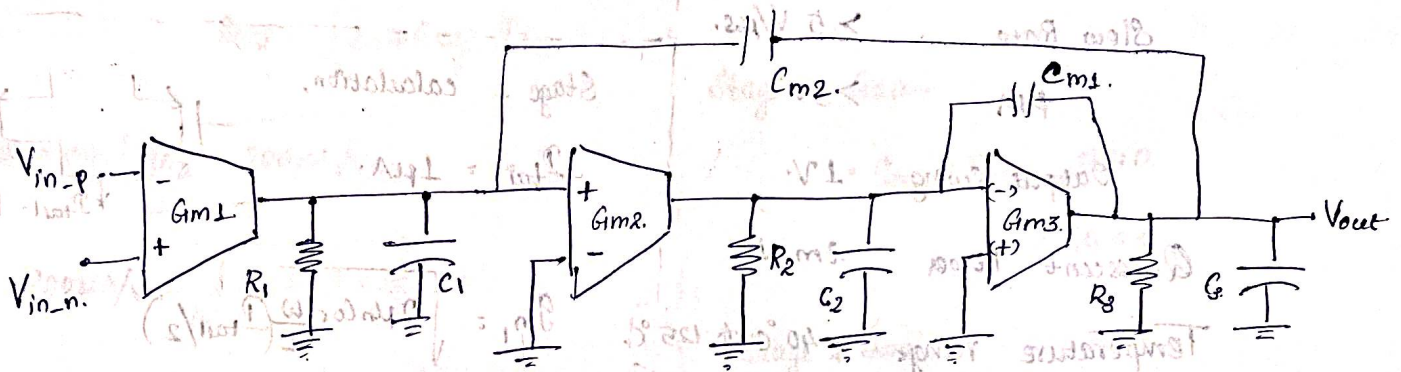



ECEN → 607 : Advanced Analog Circuit Tech.

- a) Multi-stage Op-Amp with Nested Miller Compensation.
- b) Using Cascoded Miller Compensation and Ahuja Compensation.

a) Design of 3-stage Op-amp.
Circuit Diagram.



The transistor architecture to be used:

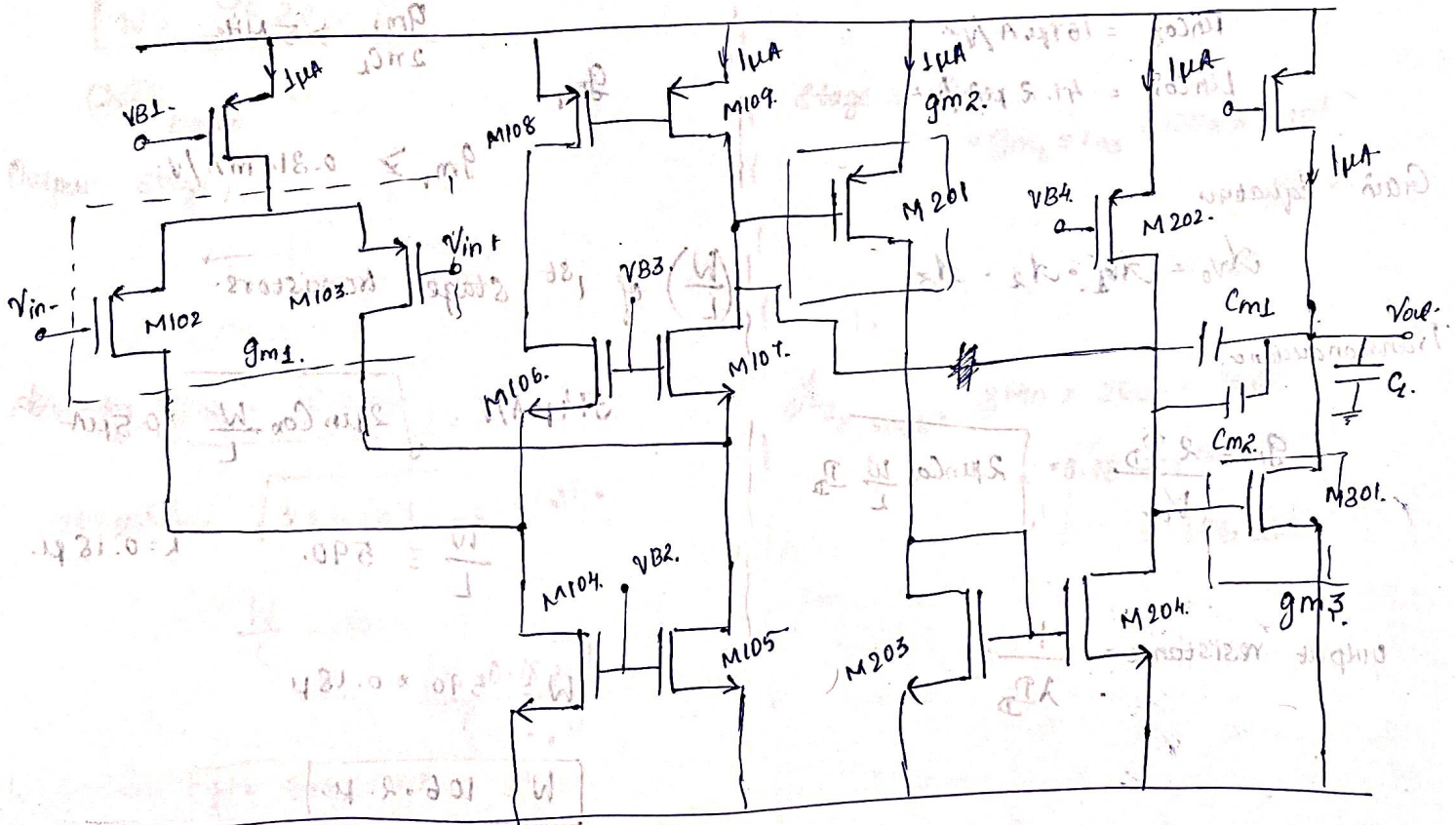

Design Specifications:-

Supply Voltage range = $1.8 \pm 5\%$

Avo. = 100dB

C load = 10pF

Unity Gain Frequency = $> 5\text{MHz}$

Slew Rate $> 5\text{V}/\mu\text{s}$

PM $> 50^\circ$

Output Swing 1V

Quiescent Power 2mW

Temperature range -40°C to 125°C

Process and Transistor Parameters:-

$\mu_n C_{ox} = 167\mu\text{A}/\text{V}^2$

$\mu_p C_{ox} = 41.2\mu\text{A}/\text{V}^2$

Gain Equation

$$A_{Vo} = A_{v1} \cdot A_{v2} \cdot A_{v3}$$

Transconductance:-

$$g_m = \frac{2I_{D1}}{V_{ov}} = \sqrt{2\mu_n C_{ox} \frac{W}{L} I_{D1}}$$

$$\text{output resistance} = \frac{1}{\lambda I_{D1}}$$

UGF

$$g_{m1}/2\pi C_L$$

$$\text{Slew rate } SR = \frac{P_{\text{stage 2}}}{C_L}$$

$$\text{Power Consumption } P = V_{DD} \times P_{\text{total}}$$

Stage 1 calculation,

$$I_{\text{tail}} = 1\mu\text{A}$$

$$g_{m1} = \sqrt{2\mu_n C_{ox} \frac{W}{L} (I_{\text{tail}}/2)}$$

UGF $> 5\text{MHz}$

$$\frac{g_{m1}}{2\pi C_L} > 5\text{MHz}$$

g_{m1}

$$g_{m1} > 0.314\text{mA}/\text{V}$$

$(\frac{W}{L})$ of 1st stage transistors

$$314\mu\text{A}/\text{V} = \sqrt{2\mu_n C_{ox} \frac{W}{L}} \times 0.5\mu\text{A}$$

$$\frac{W}{L} = 590 \quad L = 0.18\mu$$

$$W = 590 \times 0.18\mu$$

$$W = 106.2\mu$$

Stage 2:



Same current through the branch

$$I_{D2} = 1\mu\text{A}$$

$$g_{m2} = \sqrt{2\mu_n C_{ox} \frac{W}{L} I_{D2}}$$


$$\text{Assuming } g_{m2} = 200\mu\text{A}/\text{V}$$

$$200\mu\text{A}/\text{V} = \sqrt{2 \times 41.2 \times \frac{W}{L} \times 1}$$

$$\frac{W}{L} = 424$$

$$W = 46.32\mu$$

Output stage

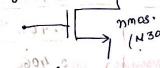

$$\text{Assuming } g_{m3} = 100\mu\text{A}/\text{V}$$

$$100\mu\text{A}/\text{V} = \sqrt{2 \times 167 \times \frac{W}{L} \times 1.8 \times 10^{-4}}$$

$$\frac{W}{L} = 30$$

$$L = 0.18\mu$$

$$W = 5.4\mu$$

$$(W/L)_{\text{pmos}} = 424$$

Gain Calculation

$$r_o = 1/\lambda I_{D1}$$

Assuming $\lambda = 0.1\text{V}^{-1}$

$$r_o = \frac{1}{(0.1)(1 \times 10^{-6})} = 10^7 \Omega$$

Stage 1 Gain =

$$= g_{m1} \times r_{o1} = 3140$$

$$= 70\text{dB}$$

Stage 2 Gain =

$$= g_{m2} \times r_{o2} = 2000$$

$$= 66\text{dB}$$

Stage 3 Gain =

$$= g_{m3} \times r_{o3} = 100\mu\text{A} \times 10^7$$

$$= 1000$$

$$= 60\text{dB}$$

$A_{Vo, \text{total}}$

$$= 3140 \times 2000 \times 1000$$

$$= 6.28 \times 10^9$$

$$= 196\text{dB}$$

Current in Each Branch:

Input pair $I_{tail} = 1\mu A$

$$I_{D1} = I_{D2} = \text{Each input transistor} = \frac{I_{tail}}{2} = 0.5\mu A$$

Slew Rate Check:


$$SR = \frac{I_{out}}{C_L} = \frac{1 \times 10^{-6}}{10 \times 10^{-12}} = 100 V/\mu s$$

Transistor	TYPE	FUNCTION / STAGE	CURRENT (μA)	W/L $1.5L = 0.18\mu$	App. V_{GS}
M101	PMOS	Bias	1	76.32 μ	0.379
M102	PMOS	Diff Pair (n-)	0.5	76.32 μ	0.385
M103	PMOS	Diff Pair (n+)	0.5	76.32 μ	0.385
M104	NMOS	Bias	1	5.40 μ	0.406
M105	NMOS	Bias	1	5.40 μ	0.406
M106	NMOS	Cascode	1	5.40 μ	0.406
M107	NMOS	Cascode	1	5.40 μ	0.406
M108	PMOS	Cascode	1	76.32 μ	0.379
M109	PMOS	Cascode	1	76.32 μ	0.379
M201	PMOS	Stage 2	1	76.32 μ	0.379
M202	NMOS	Stage 2	1	106.20 μ	0.464
M203	NMOS	Bias	1	5.4 μ	0.406
M204	NMOS	Bias	1	5.4 μ	0.406
M301	PMOS	Output Stage	1	5.4 μ	0.406
M302	PMOS	Output Stage	1	76.32 μ	0.379

2) Figure 1.2 shows a fully differential two-stage op-amp (Stage 1 is telescopic, stage 2 is common source).

Usually, the Miller caps (C_C) are connected to nodes $B+$ and $B-$. In this figure, it is connected to the cascoding nodes (A and $A+$) to mitigate the RHP zero effect and is commonly known as cascoded Miller compensation.

Circuit Diagram:-

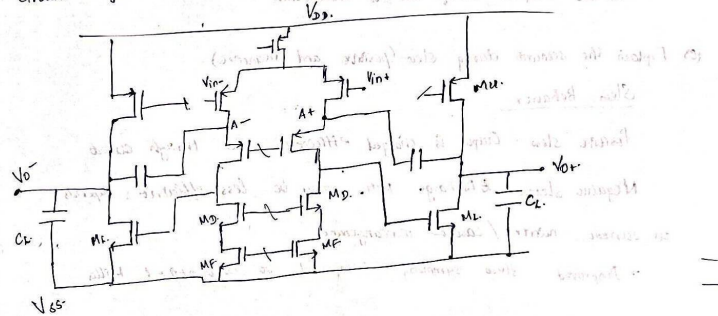

(a) How does the compensation work here? Show relevant equation -

Cascoded Miller caps connect to low-impedance cascode ($A, A+$).

The Miller capacitor current:

$$i_C = s C_m (V_m - V_{out}) \text{ produces a right-half plane (RHP) zero}$$

Araya's compensation instead injects Miller current at the cascode node:

$$i_C = s C_m V_m$$

This eliminates the $-s C_m V_{out}$ term, removing the RHP zero.

(b) Advantages and Disadvantages.

Advantages:-

- Eliminates RHP. Zero, enhancing stability
- Improves phase margin and settling.

Disadvantages:-

- More complex (needs cascode structure)
- Reduces output swing due to headroom.

(c) Explain the scenario during slew (positive and negative)

Slew Behavior:-

Positive slew: Output is charged efficiently via through cascode.

Negative slew: Discharge path, may be less efficient, depends on current mirror / cascode arrangements.

→ Improved slew symmetry compared to conventional Miller.

